

# Experiment 3 - Function Generator

Mahdi Vajhi, Seyed Alireza Mirshafiee  
810101558, 810101532

**Abstract**— The purpose of this test is to implement a function generator that can generate sine, square, etc. waves. The implementation of the sine wave is by reading the first 1/4 of it from RAM and making the rest of the wave using it. The rest of the waves are implemented using mathematical conditions and operations.

**Keywords**— Function Generator, PWM, Frequency Selector, Amplitude Selector, Digital To Analog

## I. Waveform Generator

### A. Simulation Outcomes

The simulation results of all types of waves are presented in Figure 1.

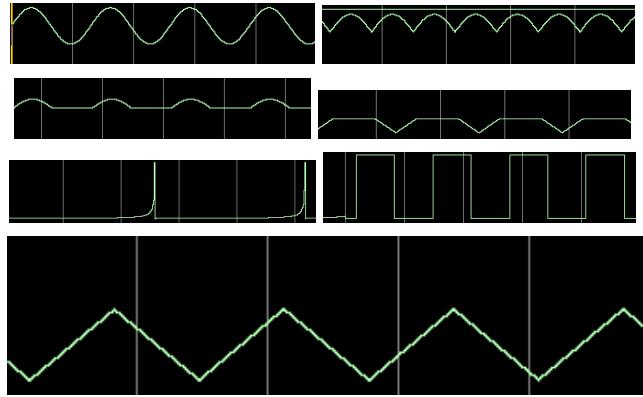


Fig. 1 Simulation Outcomes

### B. ROM

The result of circuit compilation using ROM with keyword is shown in Figure 2 and without it in Figure 3. If we do not use the keyword, the data will be logically implemented instead of being placed in the ROMs of the board.

Flow Summary	
Flow Status	Successful - Fri Jan 31 08:58:35 2003
Quartus II 32-bit Version	12.1 Build 177 11/07/2012 SJ Web Edition
Revision Name	TopModule
Top-level Entity Name	TopModule
Family	Cyclone II
Device	EP2C20F484C7
Timing Models	Final
Total logic elements	220 / 18,752 ( 1 % )
Total combinational functions	218 / 18,752 ( 1 % )
Dedicated logic registers	37 / 18,752 ( < 1 % )
Total registers	37
Total pins	14 / 315 ( 4 % )
Total virtual pins	0
Total memory bits	384 / 239,616 ( < 1 % )
Embedded Multiplier 9-bit elements	0 / 52 ( 0 % )
Total PLLs	0 / 4 ( 0 % )

Fig. 2 Compilation report for module using ROM with the romstyle keyword

Flow Summary	
Flow Status	Successful - Fri Jan 31 08:24:50 2003
Quartus II 32-bit Version	12.1 Build 177 11/07/2012 SJ Web Edition
Revision Name	TopModule
Top-level Entity Name	TopModule
Family	Cyclone II
Device	EP2C20F484C7
Timing Models	Final
Total logic elements	260 / 18,752 ( 1 % )
Total combinational functions	259 / 18,752 ( 1 % )
Dedicated logic registers	37 / 18,752 ( < 1 % )
Total registers	37
Total pins	14 / 315 ( 4 % )
Total virtual pins	0
Total memory bits	0 / 239,616 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 52 ( 0 % )
Total PLLs	0 / 4 ( 0 % )

Fig. 3 Compilation report for module using ROM without the romstyle keyword

## II. PWM

### A. Explain PWM

PWM is a module to convert digital data of our wave to analog wave. This element works in such a way that it has a 256 counter that compares in each circuit count whether the input value is greater than the counter or not. This subject causes more values of 1 to be placed on the output, and this causes the amplitude of the analog wave to increase.

## B. Simulation Results

As you can see in Figure 4, 5 and 6, PWM mode stays at 1 where the signal value is closer to 256, and this position on the analog output means more amplitude.



Fig.4 PWM for triangular wave

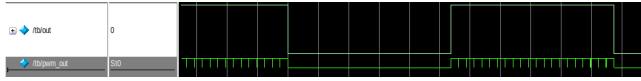


Fig.5 PWM for square wave

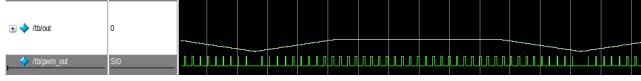


Fig.6 PWM for trapezoid wave

## III. Frequency Selector

### A. Simulation Results

The results for different values are shown in Figure 7.



Fig.7 frequency selector simulation results

## IV. Amplitude Selector

### A. Simulation Results

We tested the circuit wave amplitude for different values and you can see the result in Figure 8.

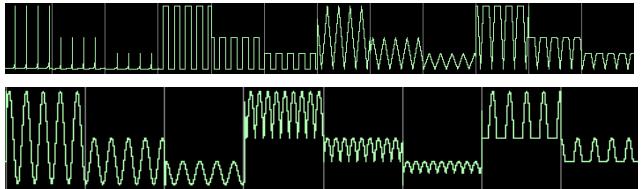


Fig.8 Simulation result for different values of wave amplitude

## V. Implementation

### A. Schematic Diagram

In Figure 9, you can see the connection schematic of the designed modules.

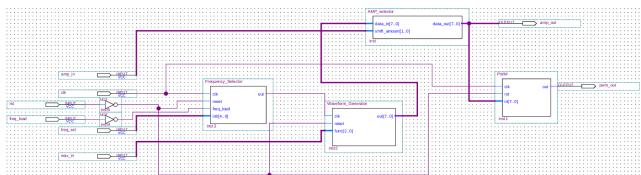


Fig.9 Schematic diagram of the Function Generator

## B. Oscilloscope Visualization

In Figure 10 to 13, you can see the effect of different amplitudes and frequencies on the sine wave, and in Figure 14, the waveforms of the remaining waves are shown.

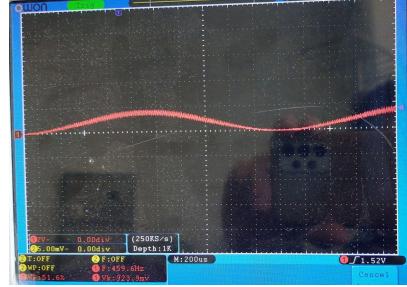


Fig.10 Sine wave with low amplitude and frequency

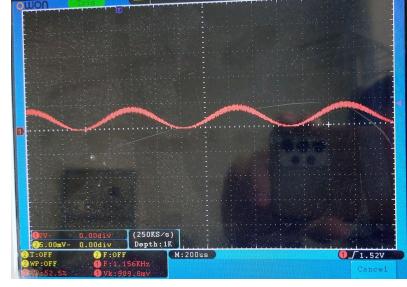


Fig.11 Sine wave with low amplitude

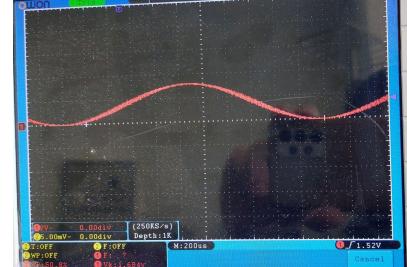


Fig.12 Sine wave with low frequency

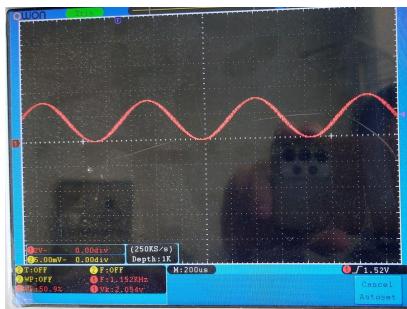


Fig.13 Normal Sine wave

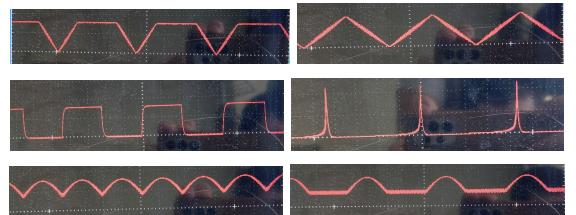


Fig.14 Other wave

## **VI. Conclusions**

In this experiment, We learned how to digitally produce a wave. We learned to convert analog signals to digital and finally we learned how to use ROM memory in an FPGA.

## **References**

- [1] K.Basharkhah, Z.Jahanpeima "Laboratory Manual, Experiment 3,Sessions 6,7,8, Clock and Periodic Signal Generation V.spring 1403" University of Tehran, College of Engineering, School of Electrical & Computer Engineering